


https://phet.colorado.edu/sims/html/capacitor-lab-basics/latest/capacitor-lab-basics_en.html

Learning Goals:

Students will be able to:

- Identify the variables that affect the capacitance and how each affects the capacitance.
- Determine the relationships between charge, voltage, and stored energy for a capacitor.
- Relate the design of the capacitor system to its ability to store energy.
- Explain how to use a capacitor to light a bulb.
- Describe what happens as charge drains away from a capacitor into a light bulb

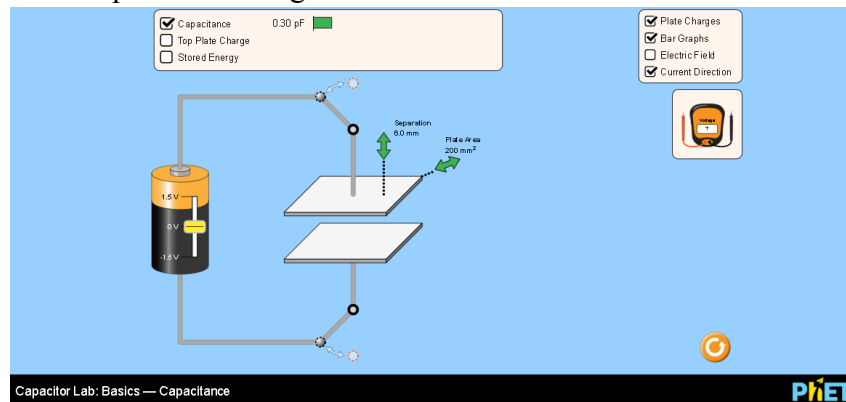
Develop your understanding: Open the [Capacitance](#) screen, then explore to develop your own ideas about how a capacitor is designed.



Explain your understanding: Use your own words and captured images from the simulation to show you can:

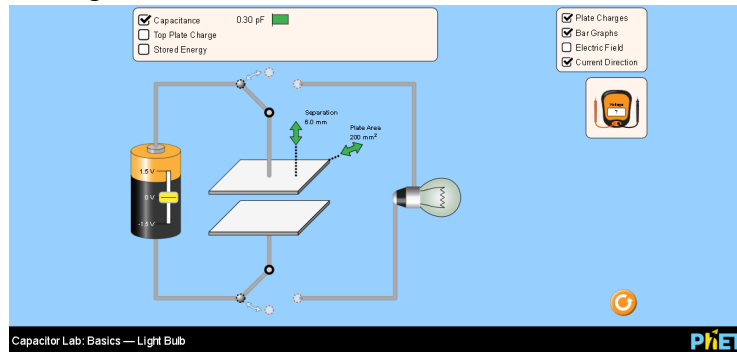
1. Identify what features of a capacitor can be maximized or minimized to make a capacitor with the greatest capacitance.
 - a. What features of the simulation did you use to help you?
2. Design experiments to find the relationships between charge, voltage, and stored energy for a capacitor. Summarize your experimental procedures and findings.
 - a. What features of the simulation did you use to help you?
3. If you wanted to design a capacitor system to store the greatest energy, what would you use?

Develop your understanding: Explore the [Light Bulb](#) screen to investigate how to use a capacitor to turn on a light bulb.



Explain your understanding: Use your own words and captured images from the simulation to show you know how to use a capacitor to light a bulb.

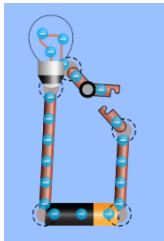4. What are the required components to use a capacitor to light a bulb and how does the system operate?
5. How would using a capacitor to light a bulb compare to using just a battery as shown:



- a. Use Circuit Construction Kit [Intro](#) screen to test your ideas and provide supporting evidence.



6. Describe what happens as charge drains away from a capacitor into a light bulb. Include the use of as many tools in the simulation as possible in your observations.
 - a. What features of the simulation did you use to help you?
7. Research to find a practical application where the energy stored in a capacitor is used. (cite references)