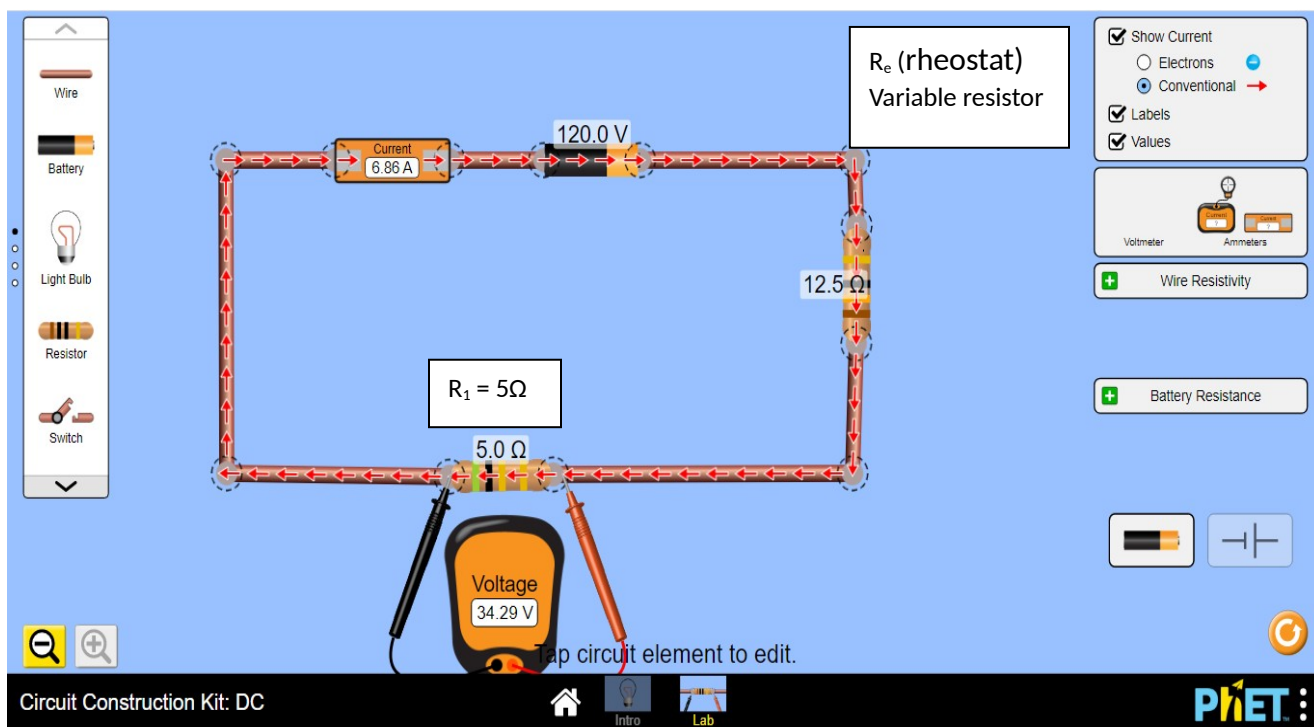



## Ohm's Law

To do the experiment by using PHET interactive simulation follow the following steps:

- 1) Click on the following link from PHET Colorado Simulation  
<https://phet.colorado.edu/en/simulation/circuit-construction-kit-dc>
- 2) Download Circuit Construction Kit: DC
- 3) Click on Lab
- 4) Choose Conventional Current
- 5) Use the components in the left side to build the circuit shown below:




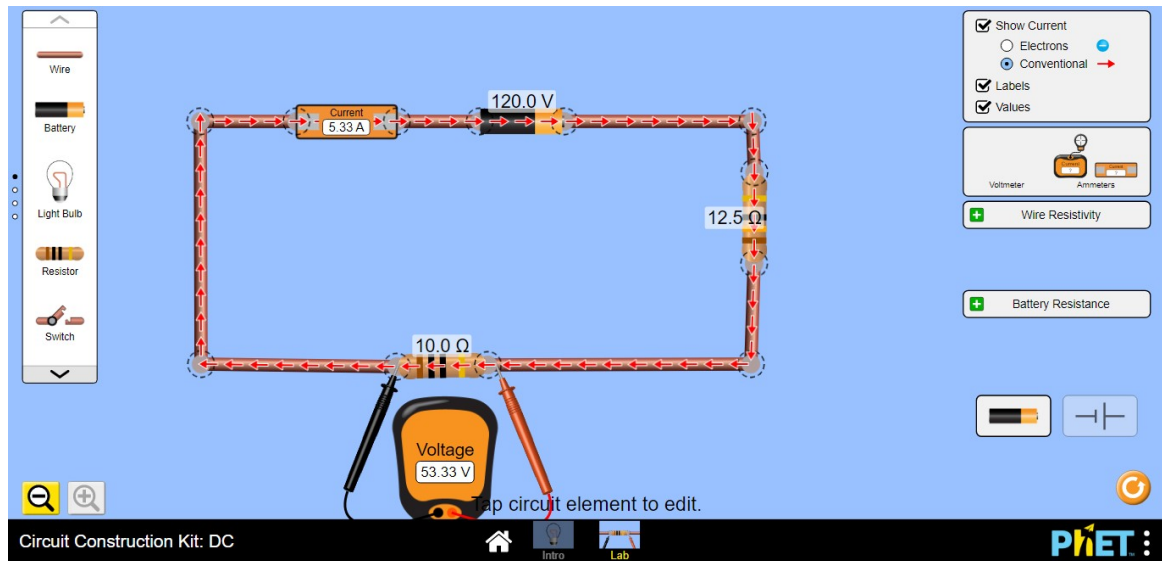- 6) Click on the resistor ( $R_1$ ) and fix it at  $5\Omega$ . That is  $R_1 = 5\Omega$ .
- 7) Click on the Battery and fix it at 120V.
- 8) Click on the Voltmeter from the right side and drag it to measure ( $V_1$ ) the voltage across  $R_1$ .
- 9) Click on the Ammeter from the right side and drag it and put it in series with  $R_1$  (before or after  $R_1$ ) to measure ( $I_1$ ).
- 10) Vary the rheostat ( $R_e$ ) to obtain 6 different readings of the electric current ( $I$ ) and the corresponding values of the voltage ( $V$ ). Then Record the values into table 1.
- 11) Replace  $R_1$  by  $R_2=10\Omega$  as shown below:




12) Again vary the rheostat ( $R_s$ ) to obtain 6 different readings of the electric current ( $I$ ) and the corresponding values of the voltage ( $V$ ). Then Record the values into table 1.

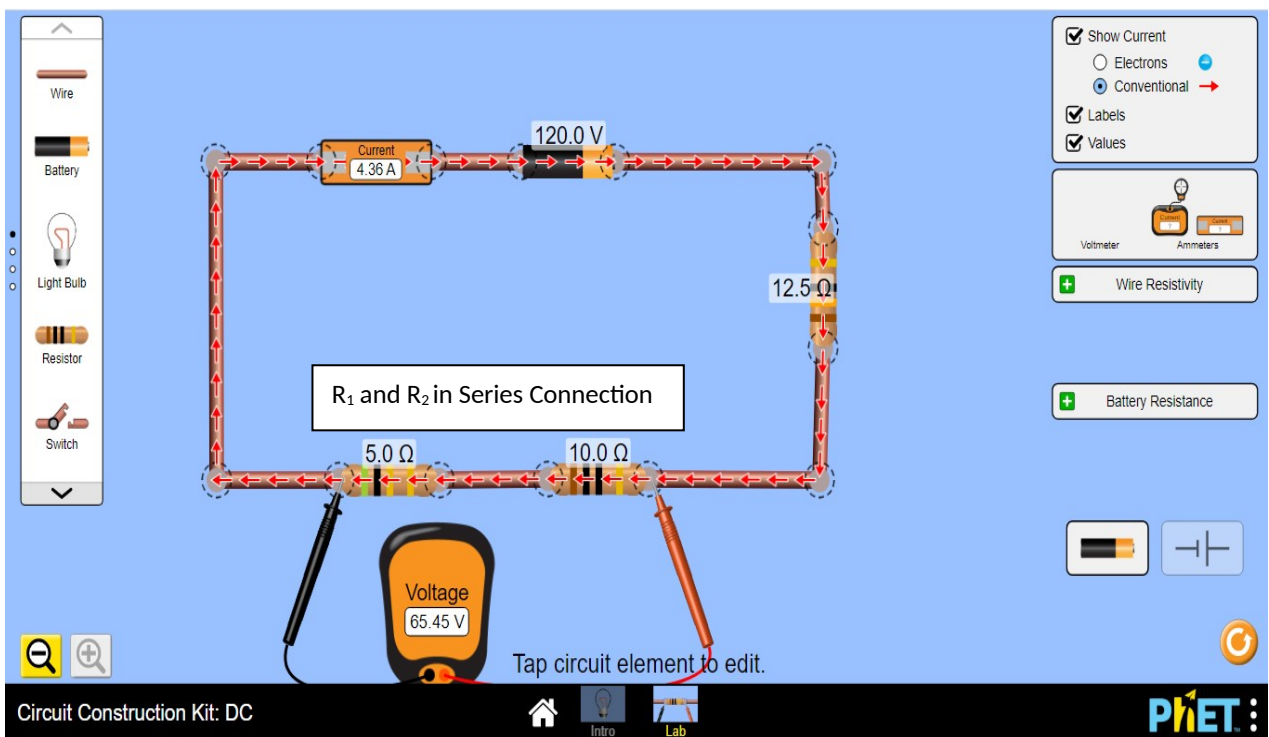13) Connect  $R_1=5\Omega$  and  $R_2=10\Omega$  in series as shown below, and again vary the rheostat ( $R_s$ ) to obtain 6 different readings of the electric current ( $I$ ) and the corresponding values of the voltage ( $V$ ). Then Record the values into table 1.



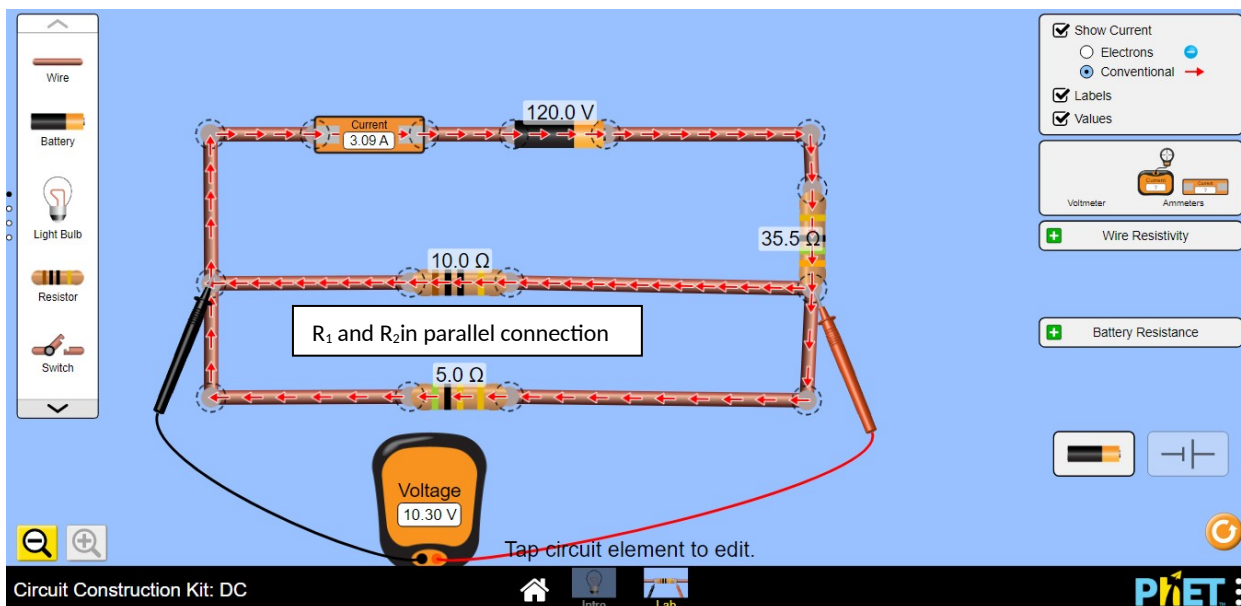14) Now connect  $R_1=5\Omega$  and  $R_2=10\Omega$  in parallel as shown below, and also vary the rheostat ( $R_s$ ) to obtain 6 different readings of the electric current (I) and the corresponding values of the voltage (V). Then Record the values into table 1.



Note that the Voltmeter is always connected in parallel with the element while the Ammeter in series

Table (1)

$R_1 (\Omega)$		$R_2 (\Omega)$		Equivalent Resistance in series		Equivalent Resistance in parallel	
V(V)	I (A)	V(V)	I (A)	V(V)	I (A)	V(V)	I (A)

- 1- Plot a graph V versus I for each case?
- 2- Does the best straight lines passes through the origin? Explain.
- 3- Calculate the slope of each graph and determine the resistance (R) from the graph (slope) and experimentally? Record the results into table 2.

**Table (2)**

	<b>Slope</b>	<b>The experimental Resistance ( <math>\Omega</math> )</b>	<b><math>\delta</math> %</b>
<b>Graph 1</b>		$R_1$ experimentally =	
<b>Graph 2</b>		$R_2$ experimentally =	
<b>Graph 3</b>		$R_{eq}$ experimentally =	
<b>Graph 4</b>		$R_{eq}$ experimentally =	

- 4- What is the difference between Ohmic resistor and a Non-Ohmic resistor?

**Ohmic:**

**Non-ohmic**

- 5- When the potential difference, V, across an ohmic resistor is increased what effect does this have on:

a. The electric current (I)

b. The resistance (R)

**Conclusions:**